
 


### Boolean Algebra & Logic gates MCQ Objective Questions:


1. The following circuit behaves as a:

 

- a) AND Gate   b) NAND Gate   c) OR Gate   **d) NOR Gate**
2. Which logic gate is represented by following circuit?




 - a) AND Gate   b) NAND Gate   c) NOT Gate   **d) OR Gate**
3. The logic function implemented in the following figure is:



- a) AND Gate   b) NAND Gate   c) NOT Gate   d) OR Gate

 
4. The symbol for two - input OR- gate in negative logic is:



5. The following gates are designated as Universal Gates

- a) NOT, OR and AND   b) XOR, OR and AND   c) XNOR, NOR and NAND   **d) NOR and NAND**

 6. The output of the logic gate in figure is



- a) 0   b) 1   **c)  $A'$**    d) A

7. The minimum number of 2-input NAND gates required to implement a 2-input XOR gate is


- a) 3   b) 5   c) 6   **d) 4**

8. The output Y of the logic circuit given below is:




- a) **1**   b) 0   c) X   d)  $X'$

 9. The output of logic circuit given below represents \_\_\_\_\_ gate.




- a) OR   b) NOR   **c) NAND**   d) AND

 10. What will be the fundamental frequency for the following circuit if each inverter delay is 100 nsec?



- a) 1GHz   b) 0.5GHz   c) 3.34MHz   **d) 1.67MHz**

 11. The minimum number of NAND gates required to realize  $AB + AB'C + AB'C'$  is  
a) 3                      b) 2                      c) 1                      **d) 0**
12. Which of the following logical operations could be computed by the given network?



- a)  $C = AB$       **b)  $C = A + B$**       c)  $C = (A.B)'$       d)  $C = (A+B)'$
13. Which of following logic gates provides output as 0 when both inputs are same (either 0 or 1)?  
a) XNOR      **b) XOR**      c) NOR      d) NAND
14. Who invented Boolean algebra?  
a) Bardeen      b) Claude Shannon      **c) George Boole**      d) None of the above
15. \_\_\_\_\_ are the methods used to represent negative integer numbers.  
a) 1's compliment      b) Sign magnitude      c) 2's compliment      **d) All of the above**
16. How many types of number systems are there?  
a) One      b) Two      c) Three      d) Four
17. The base is 16 for \_\_\_\_\_ number system  
a) Binary      **b) Hexadecimal**      c) Decimal      d) Octal
18. The American standard code for information interchange has \_\_\_\_\_ characters  
a) 64      b) 25      **c) 128**      d) None of the above
19. What is the standard form of ECDIC?  
**a) Extended Binary Coded Decimal Interchange Code**  
b) Extended Binary Coded hexadecimal Interchange Code  
c) Extended Binary Coded Decimal Information Code  
d) None of the above
20. How many types of parities are there?  
a) One      **b) Two**      c) Three      d) Four
21. The ones complement of binary number 1010 is \_\_\_\_\_  
a) 0101      b) 1010      c) 0110      d) 1110

22. The 2's complement of binary number 1010 is \_\_\_\_\_  
 a) 0101      b) 1010      **c) 0110**      d) 1110
23. The base is eight for \_\_\_\_\_ number system  
 a) Binary      b) Hexadecimal      c) Decimal      **d) Octal**
24. IC's are categorized into \_\_\_\_\_  
 a) One      **b) Two**      c) Three      d) Four  
 (Linear & digital)
25. How many gates does ultra large-scale integration contain?  
 a) 100 gates      b) 1000 gates      c) 10000 gates      **d) More than 100,000 gates**
26. How many gates does large-scale integration contain?  
 a) **100 to 10,000 gates**      b) 10,000 to 100,000 gates  
 b) 10000 gates      d) None of the above
27. The base is ten for \_\_\_\_\_ number system  
 a) Binary      b) Hexadecimal      c) Decimal      d) Octal
28. What are the advantages of ICs?  
**a) Small in size      b) Low-cost      c) Operating speed is high      d) All of the above**
29. Which IC is a quad two-input NAND gate?  
 a) 74LS00      b) 74LS01      c) 74LS03      **d) All of the above**
30. The supply voltage of the 7400 series TTL family IC's is \_\_\_\_\_  
 a) 1V      b) 2V      c) 4V      **d) 5V**
31. What is the standard form of TTL?  
 a) Transistor-Transistor Logic      b) Transistor Transducer Logic  
 b) Transducer Transistor Logic      d) None of the above
32. The voltage range of low power Schottky is \_\_\_\_\_  
 a) 1V      b) 2V      c) 4V      **d) 5V**
33. The maximum toggle speed of the 7400 TTL family ICs is \_\_\_\_\_  
**a) 20MHz**      b) 10 MHz      c) 15 MHz      **d) 25 MHz**
34. The speed of the low power Schottky is \_\_\_\_\_  
 a) 2ns      b) 8ns      **c) 10ns**      d) 12ns
35. The power of the low power Schottky is \_\_\_\_\_  
 a) 1mW      **b) 2mW**      c) 4mW      d) None of the above
36. The voltage range of advanced low power Schottky is \_\_\_\_\_  
**a) 1V**      b) 2V      c) 4V      **d) 5V**

37. The speed of the advanced low power Schottky is \_\_\_\_\_  
a) 2ns      **b) 7ns**      c) 10ns      d) 12ns
38. The power of the advanced low power Schottky is \_\_\_\_\_  
**a) 1mW**      b) 2mW      c) 4mW      d) None of the above
39. The maximum input current of the silicon gate CMOS is \_\_\_\_\_  
a) 0.1mA      b) 0.5mA      **c)  $\pm 0.0001\text{mA}$**       d) None of the above
40. The maximum clock of silicon gate CMOS is \_\_\_\_\_  
a) 20MHz      **b) 40 MHz**      c) 15 MHz      d) 25 MHz
41. The propagation time delay of the silicon gate CMOS is \_\_\_\_\_  
**a) 2ns**      b) 7ns      c) 10ns      **d) 8ns**
42. Which IC is quad two-input AND gate?  
**a) 74LS08**      b) 74LS00      c) 74LS01      d) All of the above
43. The maximum input current of the metal gate CMOS is \_\_\_\_\_  
a) 0.0001mA      **b) -0.0001mA**      c)  $\pm 0.0001\text{mA}$       d) None of the above
44. The maximum clock of the metal gate CMOS is \_\_\_\_\_  
a) 20MHz      b) 40 MHz      **c) 12 MHz**      d) 25 MHz
45. The propagation delay of the metal gate CMOS is \_\_\_\_\_  
**a) 2ns**      b) 7ns      c) 10ns      **d) 105ns**
46. How many types of logic families are there?  
**a) Two**      b) Four      c) Six      **d) Seven**
47. What is the standard form of IIL?  
a) Injection Integrated Logic      **b) Integrated Injection Logic**  
b) Integrated Integrated Logic      d) None of the above
48. The noise immunity is excellent in \_\_\_\_\_ logic family  
**a) CMOS**      b) TTL      c) ECL      d) None of the above
49. The maximum input current of the Schottky TTL gates is \_\_\_\_\_  
**a) -2.0mA**      b) 2.0mA      c) -2.5mA      d) -1.0mA
50. The maximum clock of low power Schottky TTL is \_\_\_\_\_  
a) 20MHz      **b) 40 MHz**      c) 12 MHz      d) 25 MHz
51. The propagation delay of the low power Schottky TTL is \_\_\_\_\_  
a) 2ns      b) 7ns      **c) 10ns**      d) 105ns
52. The fanout of the CMOS logic family is \_\_\_\_\_  
a) >10      b) >20      c) >30      **d) >50**

53. What are the components used in the RTL logic family?  
 a) Resistors    b) Transistors    **c) Both a and b**    d) None of the above
54. The TTL family is classified into \_\_\_\_\_  
 a) Two    **b) Four**    c) Six    d) Seven
55. Which IC is a quad two-input NOR gate?  
**a) 74LS02**    b) 74LS01    c) 74LS00    d) None of the above
56. The maximum input current of the low power Schottky TTL is \_\_\_\_\_  
 a) 0.2mA    b) 0.3mA    **c) -0.4mA**    d) 0.1mA
57. The maximum clock of Schottky TTL gate is \_\_\_\_\_  
**a) 20MHz**    b) 40 MHz    c) 12 MHz    **d) 125 MHz**
58. The fan-out of TTL logic family is \_\_\_\_\_  
 a) 2    b) 5    c) 8    **d) 10**
59. The fan-out of the ECL logic family is \_\_\_\_\_  
 c) 10    b) 20    **c) 25**    d) None of the above
60. What are the components used in the ECL logic family?  
 a) Resistors    b) Transistors    **c) Both a and b**    d) None of the above
61. In which logic family the power dissipation is very low?  
 a) RTL    b) DCTL    **c) CMOS**    d) TTL
62. Which one belongs to the unipolar logic family?  
 a) RTL, DCTL, DTL    b) TTL, ECL    **c) CMOS, PMOS, NMOS**    d) None of the above
63. The noise margin in TTL logic family is \_\_\_\_\_  
**a) Moderate**    b) Low    c) High    d) None of the above
64. The noise immunity of the CMOS logic family is \_\_\_\_\_  
 a) Poor    b) Good    **c) Very strong**    d) Strong
65. \_\_\_\_\_ are the delay of the signal transition from input to output  
**a) Propagation delay**    b) Threshold voltage  
 c) Power dissipation    d) None of the above
66. \_\_\_\_\_ is the multiplication of propagation delay and power dissipation  
 a) Propagation delay    b) Threshold voltage    c) Power dissipation    **d) Figure of merit**

